

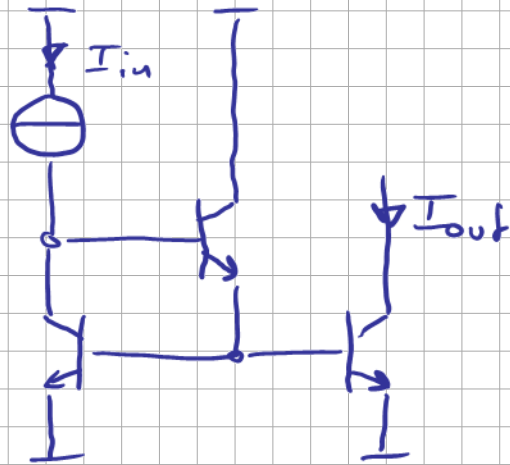


Bipolar current mirror with beta helper

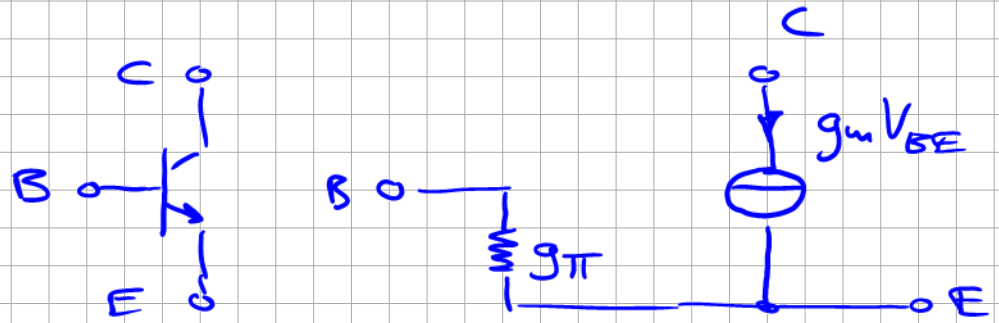


Bipolar current mirror with beta helper

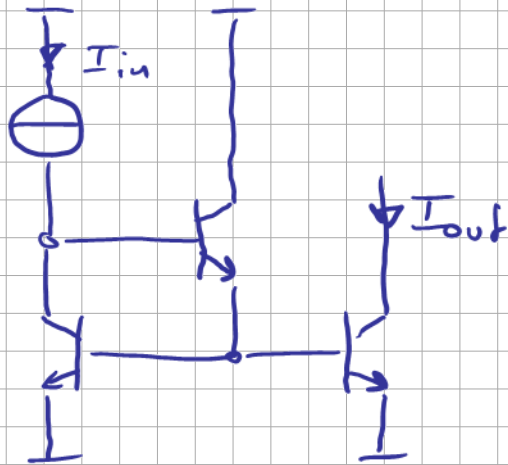


with
$$g_{\pi} = \frac{1}{\beta} \cdot g_m$$



Bipolar current mirror with beta helper

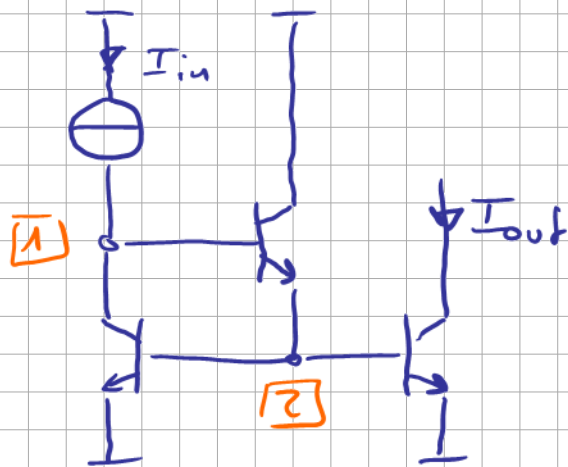
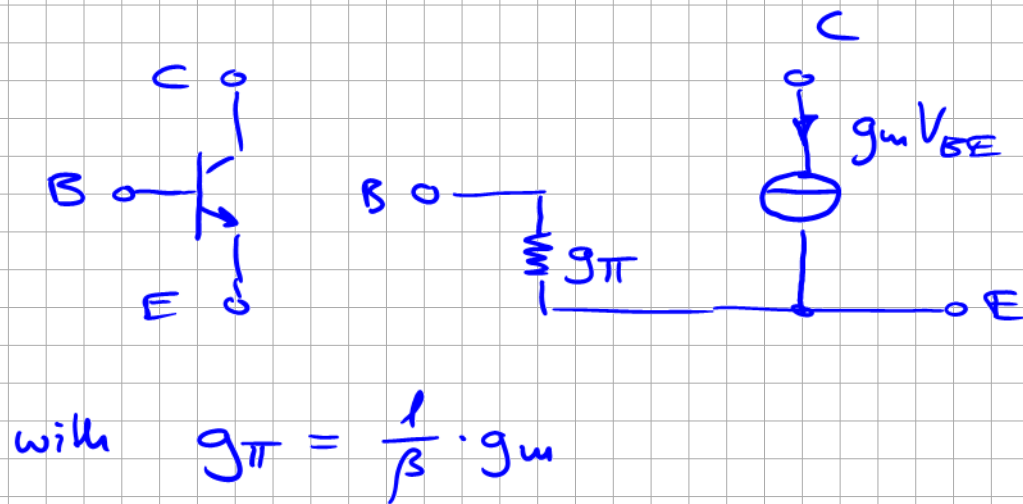
$$y_1 = \frac{1}{z_1} = g_{\pi} \quad y_2 = \frac{1}{z_2} = 3g_{\pi}$$



Bipolar current mirror with beta helper

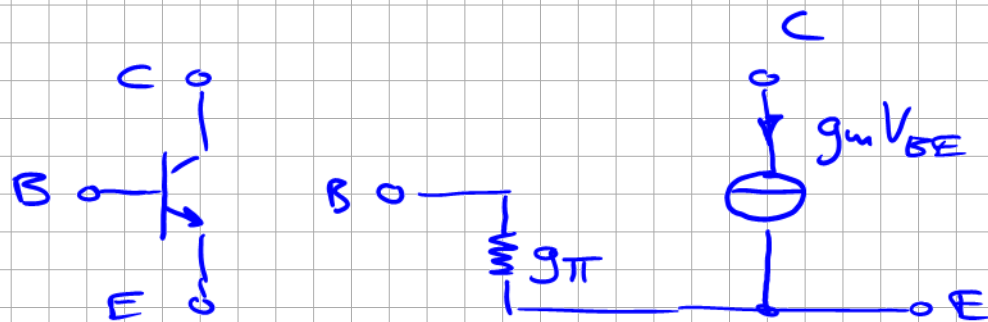
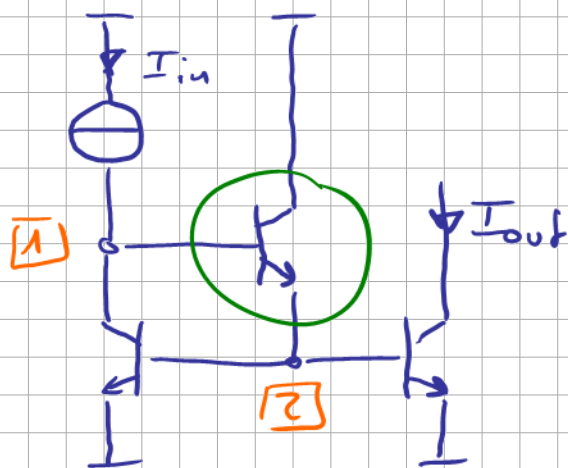


with $g_{\pi} = \frac{1}{\beta} \cdot g_m$

$$Y_1 = \frac{1}{z_1} = g_{\pi} \quad Y_2 = \frac{1}{z_2} = 3g_{\pi} + g_m$$



Bipolar current mirror with beta helper

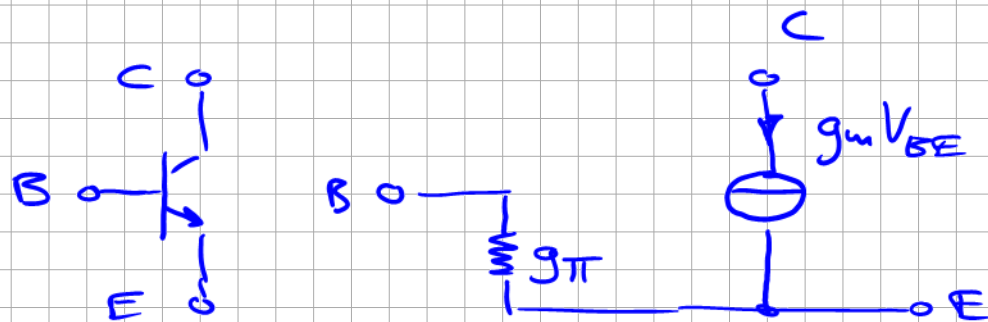
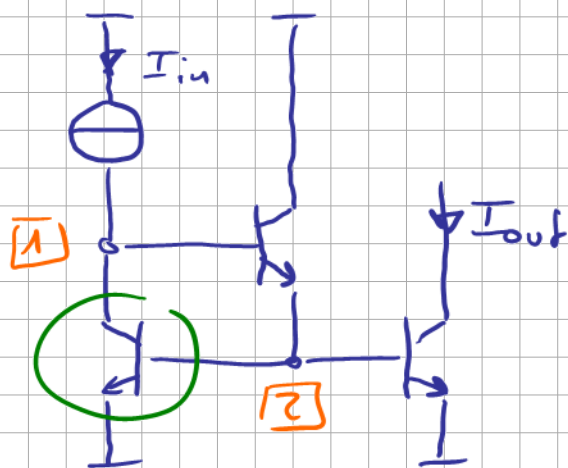


with $g_{\pi} = \frac{1}{\beta} \cdot g_m$

$$Y_1 = \frac{1}{z_1} = g_{\pi} \quad Y_2 = \frac{1}{z_2} = 3g_{\pi} + g_m$$




Bipolar current mirror with beta helper

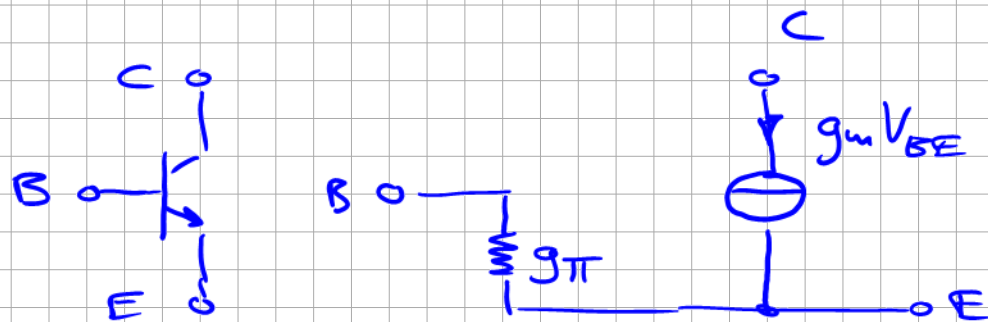
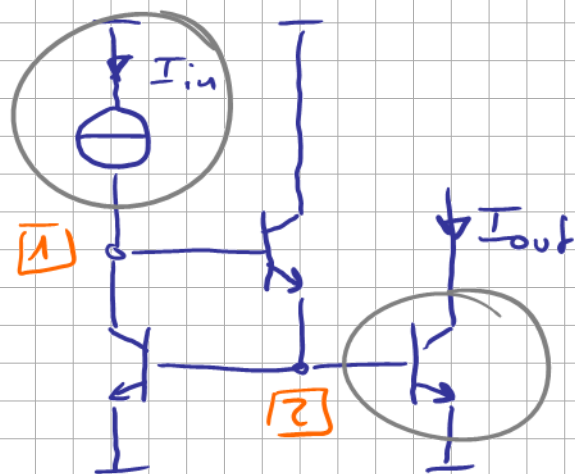


with $g_{\pi} = \frac{1}{\beta} \cdot g_m$

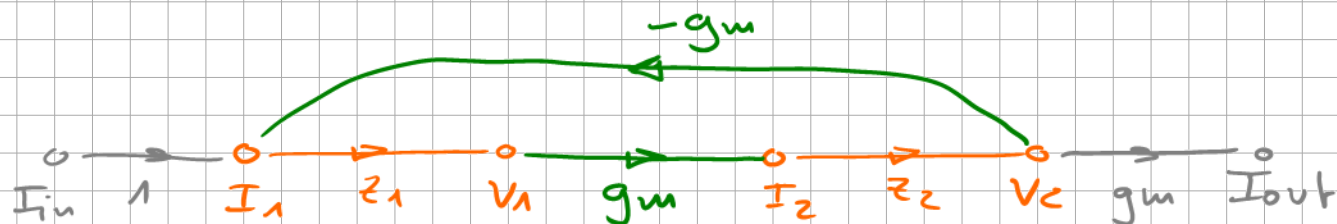$Y_1 = \frac{1}{z_1} = g_{\pi}$ $Y_2 = \frac{1}{z_2} = 3g_{\pi} + g_m$




Bipolar current mirror with beta helper

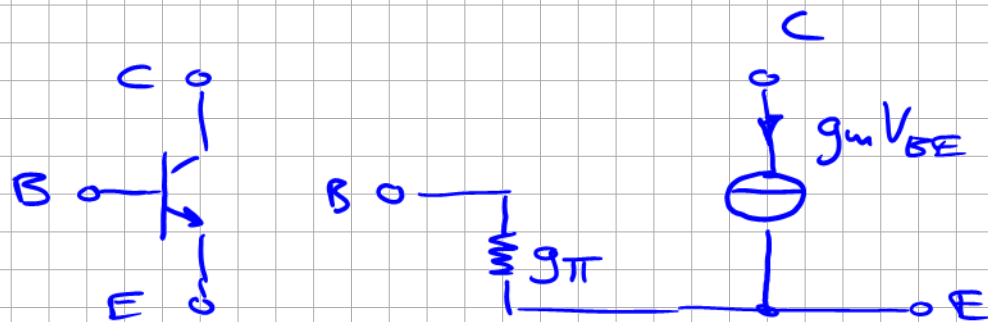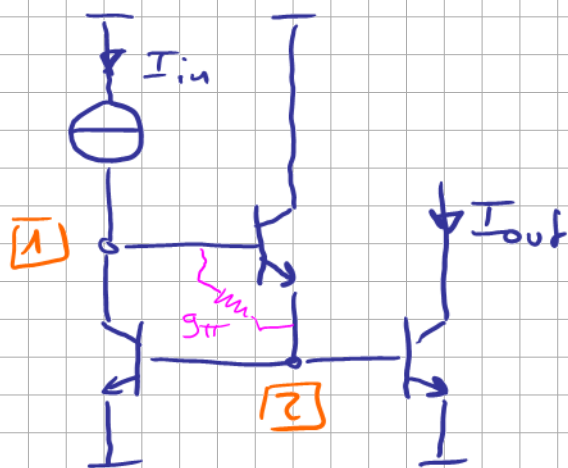


with $g_{\pi} = \frac{1}{\beta} \cdot g_m$

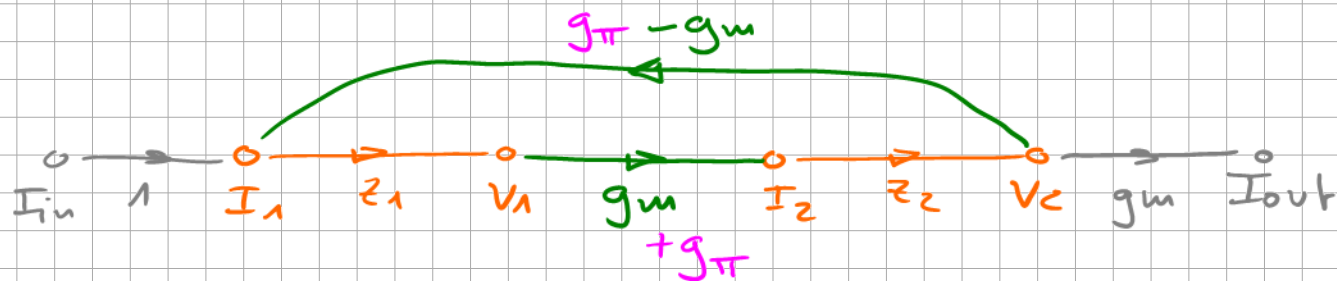$Y_1 = \frac{1}{z_1} = g_{\pi}$ $Y_2 = \frac{1}{z_2} = 3g_{\pi} + g_m$




Bipolar current mirror with beta helper

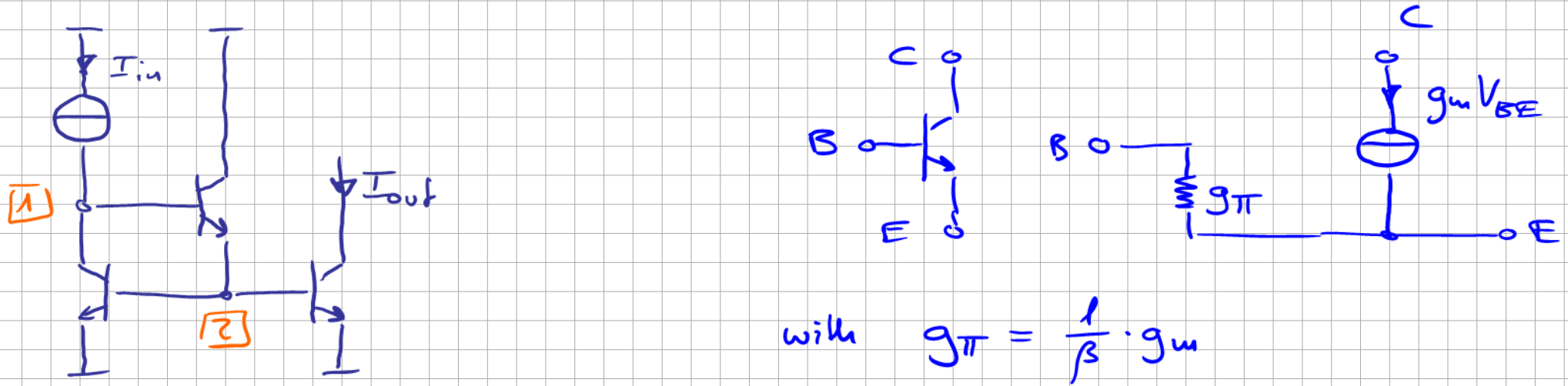

with $g_{\pi} = \frac{1}{\beta} \cdot g_m$
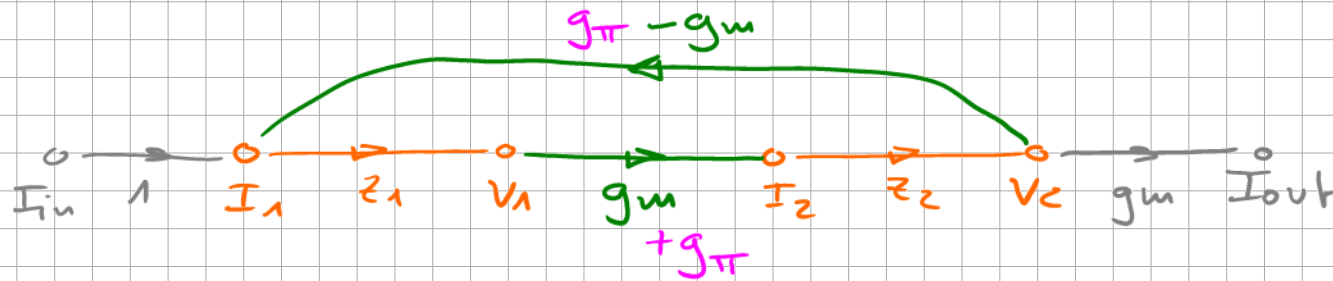
$$Y_1 = \frac{1}{z_1} = g_{\pi} \quad Y_2 = \frac{1}{z_2} = 3g_{\pi} + g_m$$





$$\begin{aligned} Y_1 Y_2 \Delta &= Y_1 Y_2 - (g_{\pi} - g_m)(g_{\pi} + g_m) = 3g_{\pi}^2 + g_{\pi} g_m - g_{\pi}^2 + g_m^2 \\ &= 2g_{\pi}^2 + g_{\pi} g_m + g_m^2 \\ &= g_m^2 \left(1 + \frac{1}{\beta} + \frac{2}{\beta^2} \right) \\ &= g_m^2 \left(1 + \frac{1}{\beta} \right) \end{aligned}$$

$$Y_1 Y_2 P_1 \Delta = g_m^2 + g_m g_{\pi}$$

$$T = \frac{I_{out}}{I_{in}} = \frac{\left(1 + \frac{1}{\beta}\right)}{\left(1 + \frac{1}{\beta} + \frac{2}{\beta^2}\right)} = \frac{\beta^2 + \beta}{\beta^2 + \beta + 2} \quad \text{E.g., } \beta = 100 \rightarrow T = \frac{10100}{10102} \approx 0.9998$$


Bipolar current mirror with beta helper

Effect of output conductance?

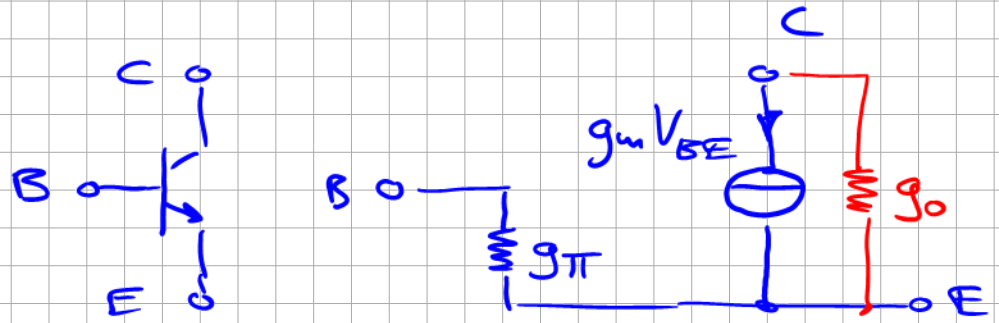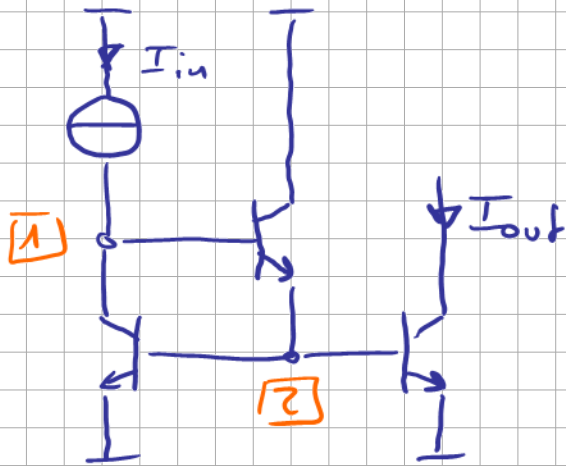

with $g_{\pi} = \frac{1}{\beta} \cdot g_m$ and $g_o = k g_m$ for some small k
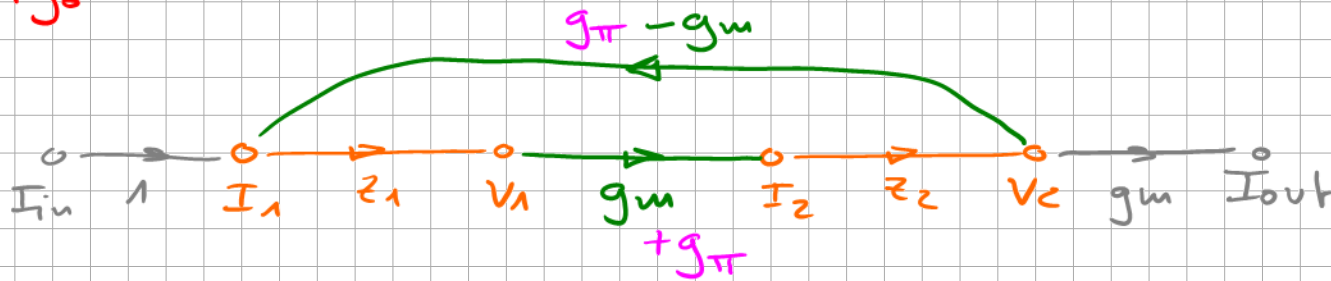
$$Y_1 = \frac{1}{z_1} = g_{\pi} + g_o \quad Y_2 = \frac{1}{z_2} = 3g_{\pi} + g_m + g_o$$



$$Y_1 Y_2 \Delta = Y_1 Y_2 - (g_{\pi} - g_m)(g_{\pi} + g_m)$$

$$= 2g_{\pi}^2 + g_{\pi}g_m + g_{\pi}g_o + 3g_{\pi}g_o + g_mg_o + g_o^2 - g_{\pi}^2 + g_m^2$$

$$= g_m^2 \left(\frac{2}{\beta^2} + \frac{1+k}{\beta} + 1 + k + k^2 \right)$$

For $4k \ll 1$, nothing really changes.

$$Y_1 Y_2 P_1 \Delta = g_m^2 + g_m g_{\pi} = g_m^2 \left(1 + \frac{1}{\beta} \right)$$

$$T = \frac{I_{out}}{I_{in}} = \frac{\left(1 + \frac{1}{\beta}\right)}{\left(1 + \frac{1}{\beta} + \frac{2}{\beta^2}\right)} = \frac{\beta^2 + \beta}{\beta^2 + \beta + 2} \quad \text{E.g., } \beta = 100 \rightarrow T = \frac{10100}{10102} \approx 0.9998$$